

Physics IV

Name:










Date:

Block:

1. Circuit Diagrams
2. Ohm's Law


Circuit Diagrams

Parts of a circuit and its connections to each other can be represented through a variety of symbols. These symbols help to indicate where each component of the circuit is placed with respect to each other.

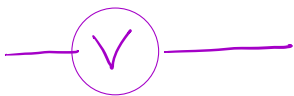
Component		Symbol	Function
Source	Cell		Provides the power source
	Battery		
Conducting Wire			Allows electricity to flow from one device to another
Resistor/Load			Controls the flow of current to other components
Switch	Open		Electrical current is off so electricity cannot pass through
	Closed		Electrical current is on so electricity can pass through
Lightbulb			A type of load that is able to change electrical energy into light and thermal energy
Ammeter			Used to measure the amount of current flowing through the circuit
Voltmeter			Used to measure the amount of voltage passing through the load

We can use these circuit symbols in order to represent how circuits are connected together.

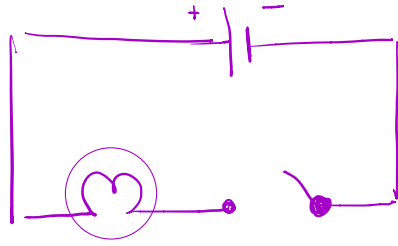
Example: Draw a circuit that has a **cell**, an **open switch** and one **light bulb** all connected in **one pathway**.



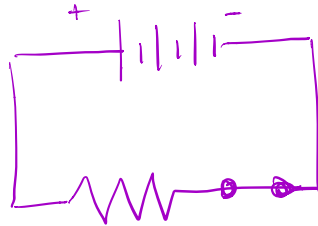Example: Draw a circuit that has a **battery**, a **closed switch** and a **resistor** connected in **one pathway**.



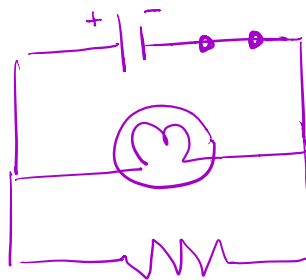Example: Draw a circuit that has a **cell** and a **closed switch** on the **main pathway**, a **light bulb** on another pathway and a **resistor** on a third pathway.



Ohm's Law

Ohm's law is formula that describes the **relationship** between **voltage**, **current**, and **resistance** in an electrical circuit.


$$V = IR$$

V = voltage (electrical potential difference) in volts (V)

I = current in amps (A)

R = resistance in ohms (Ω)

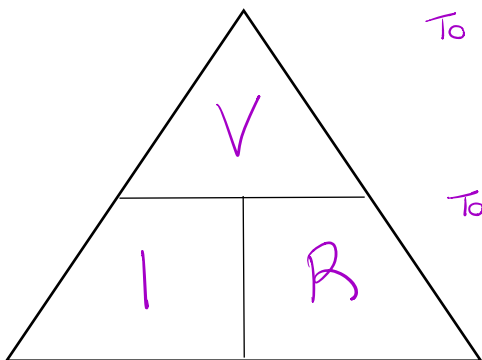We are able to **rearrange** around **Ohm's Law** in order to calculate for each of the three variables.



To find the voltage:

$$V = I \times R$$

To find resistance:

$$R = \frac{V}{I}$$

To find the current:

$$I = \frac{V}{R}$$

Example: The filament of a light bulb has a resistance of 20.0 Ω. A 5.0 V battery is used in the circuit. What is the current?

Step 1: Identify the known values

① $R = 20.0 \Omega$

② $I = V/R$

Step 2: Write the equation

$V = 5.0V$

③ $I = \frac{5.0V}{20.0\Omega}$

$I = ?$

④

Step 3: Replace the known values

Step 4: Solve

⑤ $I = 0.25A$

Step 5: Label with units

**Do NOT forget the units!!!*

Example: If the current of a circuit is 10.0 A and voltage from the battery is 20.0 V. How much resistance is needed in the load?

Step 1: Identify the known values

$I = 10.0A$

$R = \frac{V}{I}$

Step 2: Write the equation

$V = 20.0V$

$R = \frac{20.0V}{10.0A}$

Step 3: Replace the known values

$R = ?$

$R = 2.0\Omega$

Step 4: Solve

Step 5: Label with units