

**STATION 1**  
VOCABULARY

Make sure you know what each of these words mean. If you know, check the box. If you don't, ask someone in your group and write down the definition

- Potential energy:
- Kinetic energy:
- Law of electric charge:
- Source:
- Conductor:
- Load/Resistor:
- Switch:
- Current:
- Electrical Potential Difference:
- Resistance:
- Short circuit:
- Insulator:
- Series Circuit:
- Parallel Circuit:
- Phantom load:
- Generating electrical energy:

**STATION 1**  
VOCABULARY

Make sure you know what each of these words mean. If you know, check the box. If you don't, ask someone in your group and write down the definition

- Potential energy:
- Kinetic energy:
- Law of electric charge:
- Source:
- Conductor:
- Load/Resistor:
- Switch:
- Current:
- Electrical Potential Difference:
- Resistance:
- Short Circuit:
- Insulator:
- Series Circuit:
- Parallel Circuit:
- Phantom load:
- Generating electrical energy:

**STATION 2**  
DRAWING CIRCUIT DIAGRAMS

Draw a circuit diagrams for the following circuits. Be sure to identify the direction that current is travelling for each scenario.

1. A circuit with a cell that runs a buzzer.
  
  
  
  
  
  
  
  
  
  
2. A circuit with a battery where an open switch has turned off two lights placed in parallel to each other.
  
  
  
  
  
  
  
  
  
  
3. A circuit with a battery, a closed switch, two light bulbs, and a clock all in series with each other.
  
  
  
  
  
  
  
  
  
  
4. A circuit with an electrochemical cell, a closed master switch, and three light bulbs all in parallel with each other. Each light bulb has its own switch that turns it on and off.

**STATION 2**  
DRAWING CIRCUIT DIAGRAMS

Draw a circuit diagrams for the following circuits. Be sure to identify the direction that current is travelling for each scenario.

1. A circuit with a cell that runs a buzzer.
  
  
  
  
  
  
  
  
  
  
2. A circuit with a battery where an open switch has turned off two lights placed in parallel to each other.
  
  
  
  
  
  
  
  
  
  
3. A circuit with a battery, a closed switch, two light bulbs, and a clock all in series with each other.
  
  
  
  
  
  
  
  
  
  
4. A circuit with an electrochemical cell, a closed master switch, and three light bulbs all in parallel with each other. Each light bulb has its own switch that turns it on and off.

**STATION 3**  
CALCULATING OHM'S LAW

	Symbol	Unit
Current		
Voltage		
Resistance		

1. What is the resistance of a toaster if a current of 12.5 A flows through it when it is connected to 120 V?
  
  
  
  
  
  
  
  
  
  
2. A light bulb has a resistance of 90  $\Omega$ . What current flows through the bulb when it is connected to 120 V?
  
  
  
  
  
  
  
  
  
  
3. The current through a load in a circuit is 2.5 A. If the voltage is 75 V, what is the resistance of the load?
  
  
  
  
  
  
  
  
  
  
4. How much electrical potential difference is necessary to generate 9.5 A in a circuit with 2.0  $\Omega$ ?

**STATION 3**  
CALCULATING OHM'S LAW

	Symbol	Unit
Current		
Voltage		
Resistance		

1. What is the resistance of a toaster if a current of 12.5 A flows through it when it is connected to 120 V?
  
  
  
  
  
  
  
  
  
  
2. A light bulb has a resistance of 90  $\Omega$ . What current flows through the bulb when it is connected to 120 V?
  
  
  
  
  
  
  
  
  
  
3. The current through a load in a circuit is 2.5 A. If the voltage is 75 V, what is the resistance of the load?
  
  
  
  
  
  
  
  
  
  
4. How much electrical potential difference is necessary to generate 9.5 A in a circuit with 2.0  $\Omega$ ?

**STATION 4**

**ENERGY SOURCES AND TRANSFORMATIONS**

Identify the type of energy associated with each of the following sources:

- a. The Sun
- b. River flow
- c. A battery
- d. Uranium
- e. Food

	<b>ORIGINAL ENERGY FORM</b>	<b>FINAL ENERGY FORM</b>
Photosynthesis		
Nuclear power plant		
An oven		

List the three key parts of a generator system. Briefly describe their functions

What is the difference between a renewable and non-renewable energy source? Provide at least 2 examples for each.

**STATION 4**

**ENERGY SOURCES AND TRANSFORMATIONS**

Identify the type of energy associated with each of the following sources:

- a. The Sun
- b. River flow
- c. A battery
- d. Uranium
- e. Food

	<b>ORIGINAL ENERGY FORM</b>	<b>FINAL ENERGY FORM</b>
Photosynthesis		
Nuclear power plant		
An oven		

List the three key parts of a generator system. Briefly describe their functions

What is the difference between a renewable and non-renewable energy source? Provide at least 2 examples for each.